



Internal resistance of the PCB is 5k so the 390R is to trim the output of the joystick to get the centre point of the 4.1V - 1.1V range to 2.65V (as the Ecorider uses) allowing that the Ecorider uses 5.1 V as a supply, not the 5V specified